

Name (Pin Yin): Solution

CQUPT EE310 2020 Fall Quiz 3a


(15min, 20pts)

1. (4pts) For a 7-seg LED display, all outputs are active HIGH.
- a. Write the input binary code to display the hexadecimal number 'E'.

1110

- b. What is the logic level for each output in order of abcdefg?

1001111

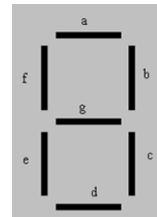

2. (6pts) Read the following System Verilog program and answer the questions.

- a. How many input and output ports in the module named dec1?

1 input port and 1 output port

- b. How many input and output pins in this circuit?

2 input pins, 4 output pins

- c. Describe the function of the logic circuit. If possible, write down the official name of this circuit.

This circuit functions as an encoder whose output is the binary equivalent of a power of 2 specified by the input, I.

```
module dec1 (input logic [1:0] I,
             output logic [3:0] O);
    always @(I)
    begin
        case(I)
            2'b00: O = 4'b0001;
            2'b01: O = 4'b0010;
            2'b10: O = 4'b0100;
            2'b11: O = 4'b1000;
            default: O = 4'bxxxx;
        end case;
    end
endmodule
```

3. (6pts) Rewrite the always block in question 2 using if –else if – else statements.

```
always @(I)
begin
    if(I == 2'b00) O = 4'b0001;
    else if(I == 2'b01) O = 4'b0010;
    else if(I == 2'b10) O = 4'b0100;
    else if(I == 2'b11) O = 4'b1000;
    else O = 4'bxxxx;
end
```

4. (4pts) A signal is defined as logic type, please explain what the following values mean.

'1': Logic level high or true or 1

'0': Logic level low or false or 0

'z': High Impedance (no connection)

'x': Logic level unknown

Name (Pin Yin): Solution

CQUPT EE310 2020 Fall Quiz 3b

(15min, 20pts)

1. (4pts) For a 7-seg LED display, all outputs are active LOW.
 - a. Write the input binary code to display the hexadecimal number 'C'.
1100
 - b. What is the logic level for each output in order of abcdefg?
1001110
2. (6pts) Read the following System Verilog program and answer the questions.
 - a. How many input and output ports in the module named mux4?
Two input ports, One output port
 - b. How many input and output pins in this circuit?
Six input pins, One output pin
 - c. Describe the function of the logic circuit. If possible, write down the official name of this circuit.
This is a 2 by 4 multiplexer that by way of the sel input, select one of four input lines to send to the output.

```
module mux4 (input logic [3:0] d_in,
             input logic [1:0] sel,
             output logic O);
);
    always @(sel, d_in)
    begin
        case(sel)
            2'b00: O = d_in[0];
            2'b01: O = d_in[1];
            2'b10: O = d_in[2];
            2'b11: O = d_in[3];
        end case;
    end
endmodule
```

3. (6pts) Rewrite the always block in question 2 using if –else if- else statements.

```
always @(sel, d_in)
begin
    if(sel == 2'b00) O = d_in[0];
    else if(sel == 2'b01) O = d_in[1];
    else if(sel == 2'b10) O = d_in[2];
    else if(sel == 2'b11) O = d_in[3];
end
```

4. (4pts) A signal is defined as logic type, please explain what the following values mean.

'X': Unknown logic level

'1': Logic level high or true or 1

'0': Logic level low or false or 0

Z': High Impedence (no connection)